

COA UPE

VISHAL KUMAR

RA1911026010052


Alloted question No-(26)

Q1.) Implement Carry Save Multiplier for 3 bit input.

AIM: To design and implement a Carry save multiplier for 3 bit input.

SOFTWARE: Logic gate simulator

Circuit diagram:-

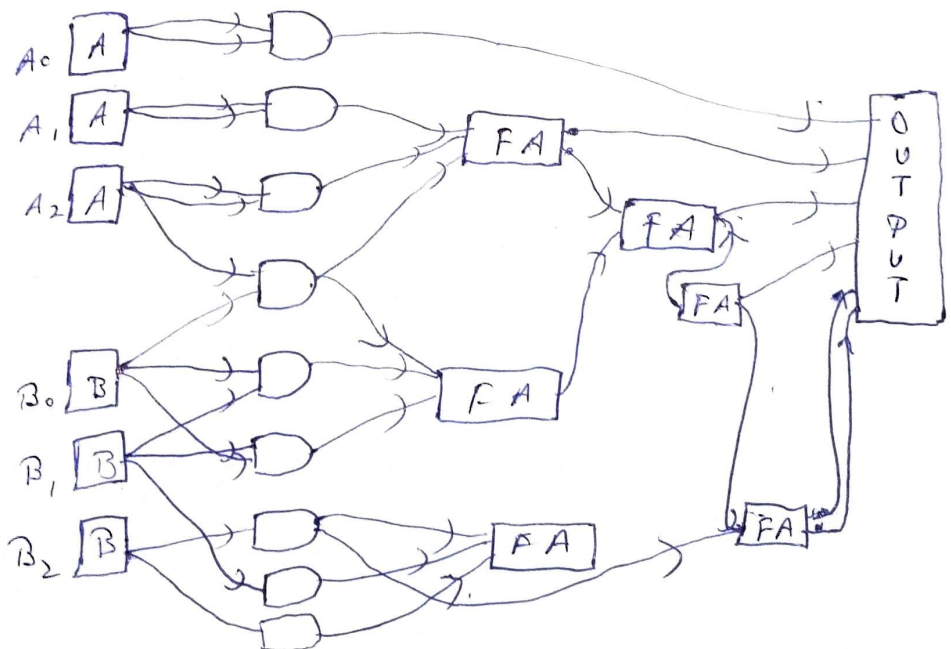

## Procedure

- open logic gate simulator
- create a full adder circuit first
- Then create an IC using the full adder circuit
- Now open a new file in logic gatesim
- Take 6 user inputs and place as given in circuit diagram.
- And using AND gates of total 9 and give connection.
- Now export IC of full adder and place it in circuit connection.  
A total of 6 full adder IC must be used
- Now for output select numeric output and give 6 pin connection.
- Give proper connections.

TRUTH TABLE :- (Keeping  $A_0 = 1$ ,  $A_1 = 1$ )

$A_0$	$A_1$	$A_2$	$B_0$	$B_1$	$B_2$	Output
1	0	0	1	0	0	1
1	0	0	0	1	0	2
1	0	0	0	0	1	4
1	0	0	1	1	0	3
1	0	0	0	1	1	6
1	0	0	1	0	1	5
1	0	0	1	1	1	7
0	1	0	1	0	0	2
0	1	0	0	1	0	4
0	1	0	0	0	1	8
0	1	0	1	1	0	6
0	1	0	0	1	1	C
0	1	0	1	0	1	A
0	1	0	1	1	1	F

Q2.) Subtraction of 2 numbers in 8086

Algorithm:-

data segment

A db 0Fh

B db 0Ch

data ends

Code segment

assume CS: code, ds: data

Start:

mov ax, data

mov ds, ax

mov al, A

mov bl, B

sub al, bl

mov cx, ax


Code ends


end start


## Algorithm:

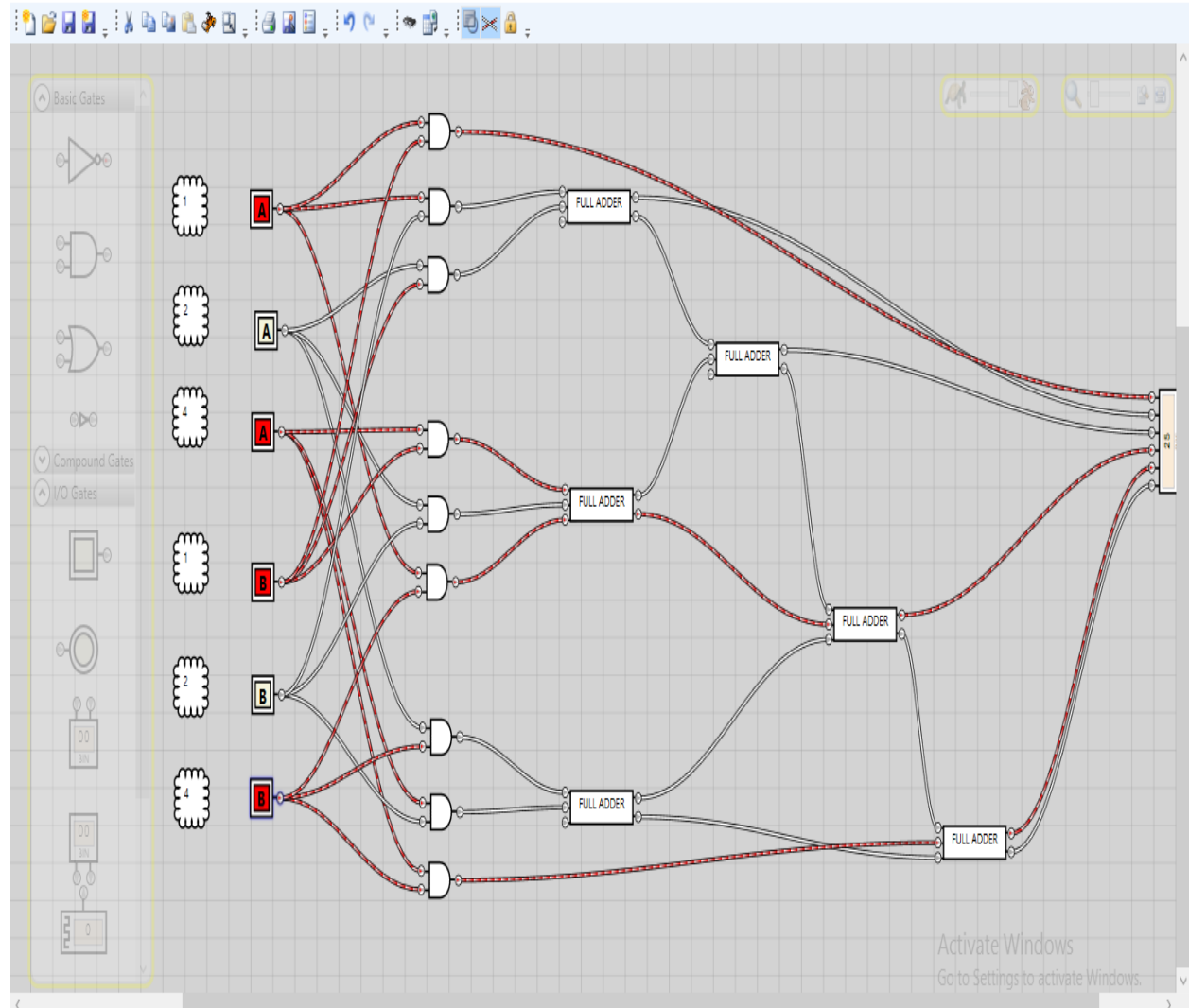- 1.) Load data to register AL (1<sup>st</sup> No)
- 2.) Load data to register BL (2<sup>nd</sup> No)
- 3.) Subtract these two numbers  
(contents of register AL and register BL)
- 4.) Apply DAS instruction (decimal adjust)
- 5.) Store result (content of AL)
- 6.) Set register AL to 00
- 7.) Add contents of register AL  
to itself with carry (b00000)
- 8.) Store the result (content of register AL)
- 9.) Stop





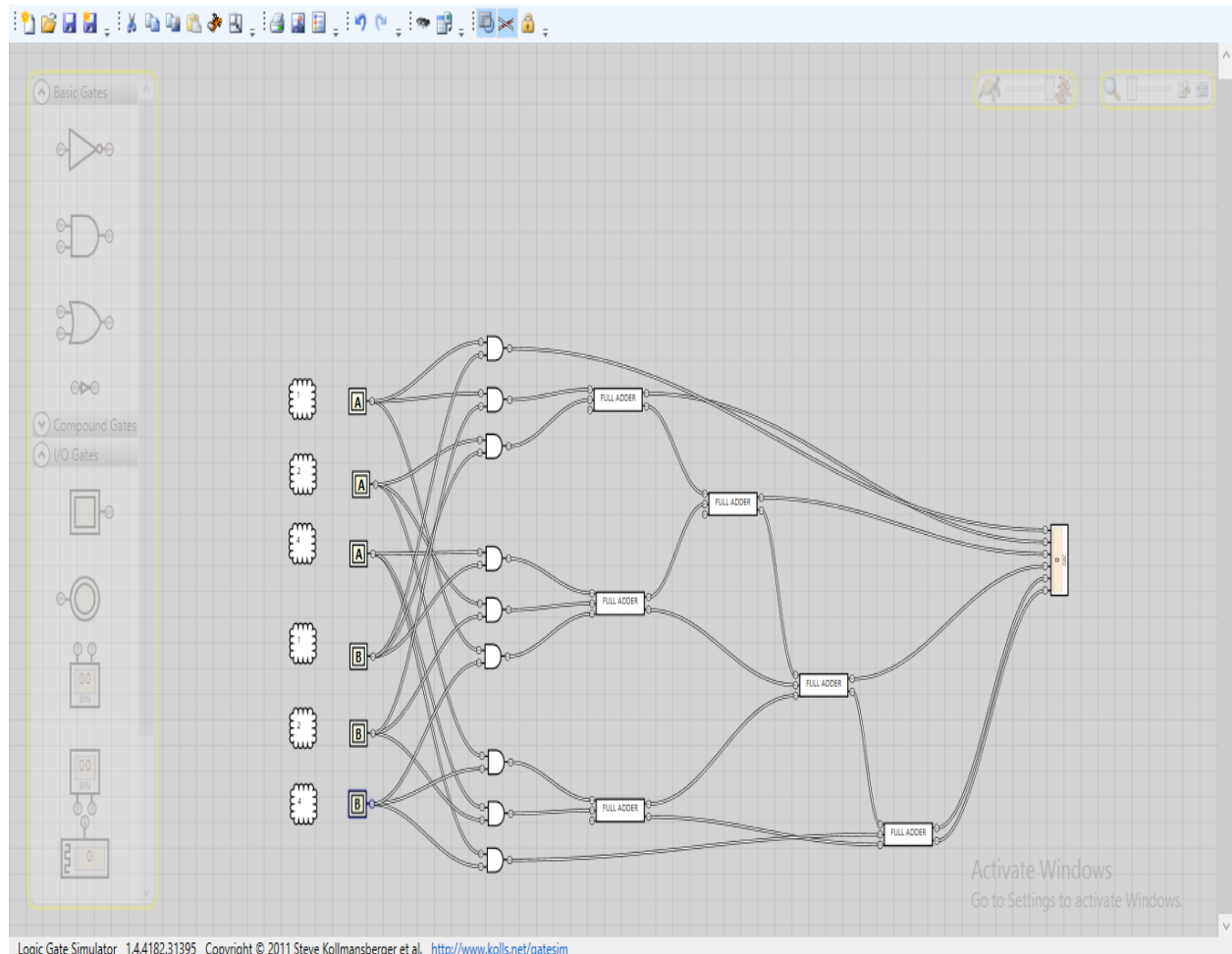

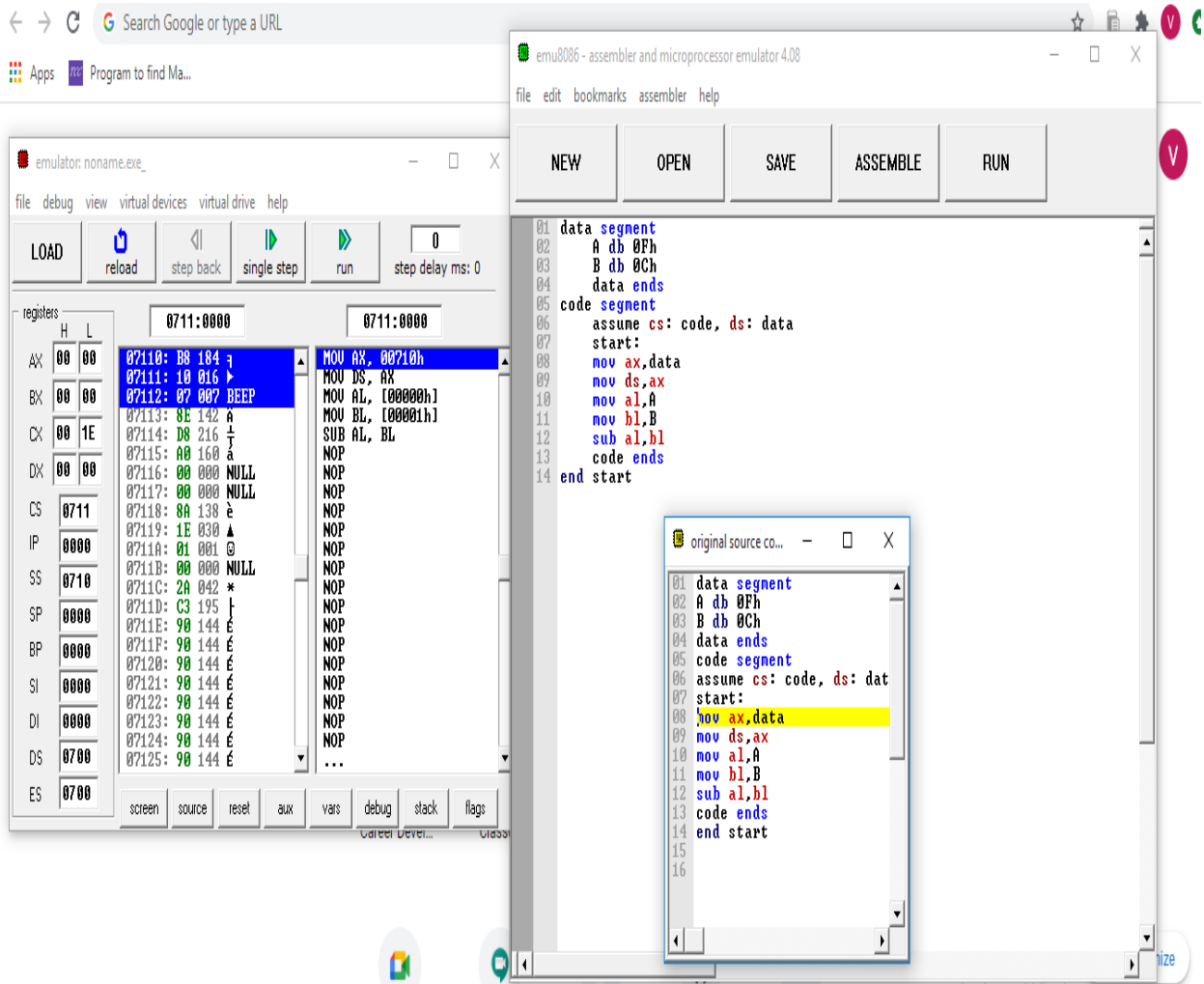



Hence Subtraction of two 8 bit Numbers are done.